EC3091D - Experiment 8

Bistable - Trial 1 / Figure 4

R = 100 ohm; C = 0.1 uF; supplies = +/-15 V

NATIONAL SEMICONDUCTOR LM741 MACROMODEL

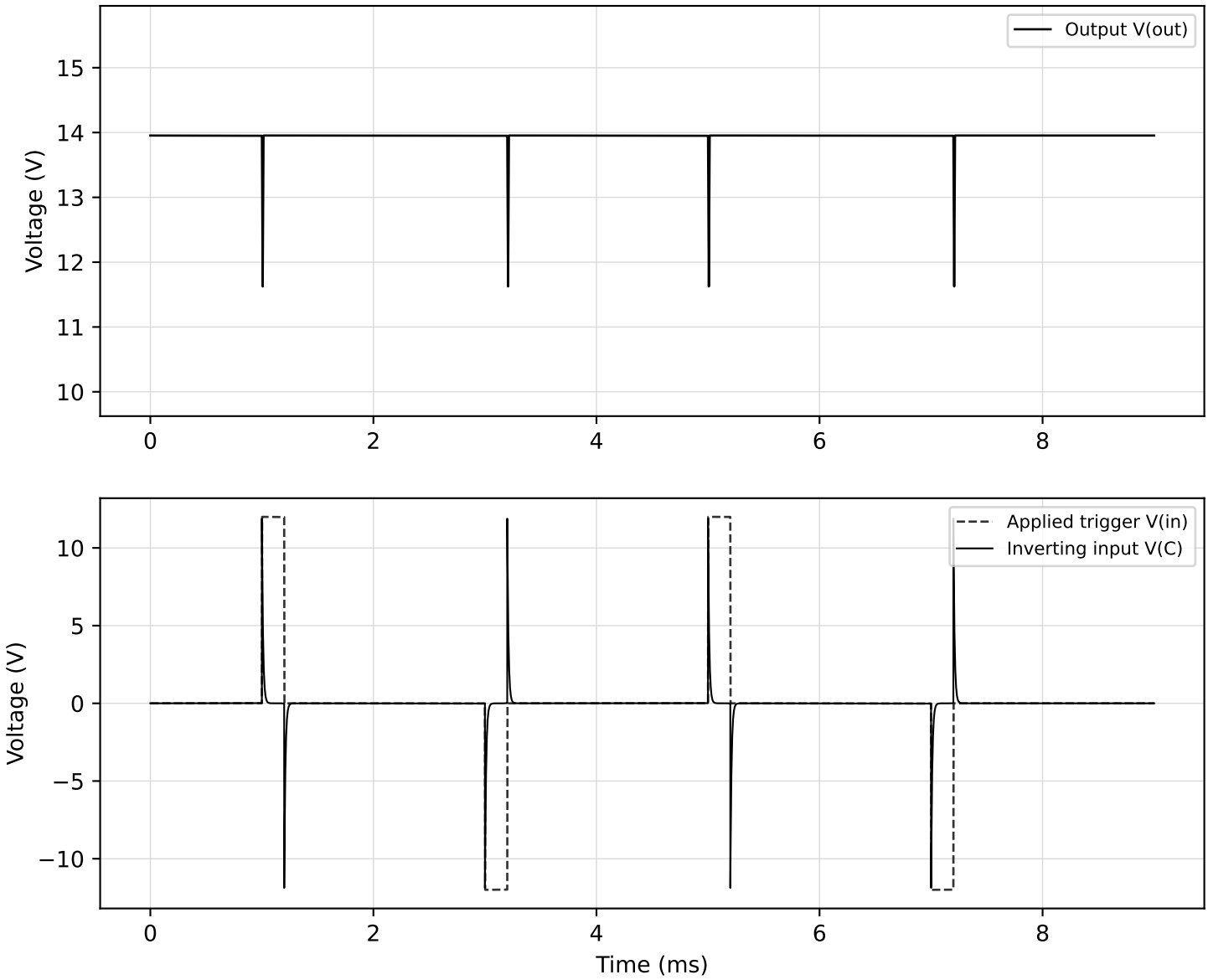

FAIL: output did not switch with the specified trigger. f, T, duty: N/A

Measured from ngspice numerical transient data; 0 V output crossings.

Data: simulation_data/bistable_01.txt

Observation / handwritten notes: _____

_____